



$$\text{Total delay} = D = N \text{ fan } \delta$$

driver sees this \rightarrow C_{load}

Ratio = $\frac{C_{in, next}}{C_{gate, min}} = \text{fan } N = \left(\frac{C_{load}}{C_{in}} \right)$

call it $\rightarrow R$ \rightarrow smallest gate \rightarrow fan out \rightarrow no of stages

$$\text{fan out} = \frac{I_o}{I_i} \Rightarrow \frac{W_i}{W_{i-1}}$$

now write an equation to minimize total delay as a function of # of stages

$$\frac{\partial}{\partial N} (NR^{1/N}\delta) = R^{1/N}\delta + N\delta \frac{\partial}{\partial N} (R^{1/N})$$

$$= R^{1/N}\delta + \frac{N\delta \ln(R)}{N^2} R^{1/N}$$

minimize

$$0 = R^{1/N}\delta \left(1 - \frac{\ln R}{N} \right)$$

$$\frac{\ln(R)}{N} = 1$$

$$\text{no of stages } N = \ln(R)$$

$$\frac{C_{in}}{C_{gate}^{min}}$$

Example

$$C_{in} = 0.1 \text{ pF}$$

$$\text{last stage } C = 5 \text{ pF}$$

solve

$$R = e^N$$

$$f_{an} = R^{1/N}$$

$$f_{an} = (e^N)^{1/N} = e$$

$$\frac{0.1 \text{ pF}}{5 \text{ pF}} = \frac{1}{50} = -3.192 \Rightarrow 4 \text{ stages}$$

Each stage is successively wider

$$\text{fan out} = \frac{I_{out}}{I_{in}} = \frac{W_i}{W_{i-1}}$$

$$\text{optimum fan out is } f_{an} = e = 2.718$$

but we will typically use an integer
(standard cell)

this analytical solution is good but treats
each inverter as perfect with no capacitance

so now solve this problem in Hspice